


# The Challenge of Future Energy Systems: Analysis of the Voltage Drop in Transmission Lines

Date: April 26th, 2017

Authors: *Gonzalo Sánchez Contreras, Emilio de las Heras Páez de la Cadena, Ignacio Sanz Soriano*

**Objective:** The aim of this notebook is to analyze and compare transmission line simulation results with the real measures obtained in the laboratory in different load scenarios to study the effects on voltage, current and losses. To achieve these goal, we use a scale transmission line to take measures that are then rescaled to real ones (132 kV, 100 MVA) and compare with simulation results using distributed parameters model.
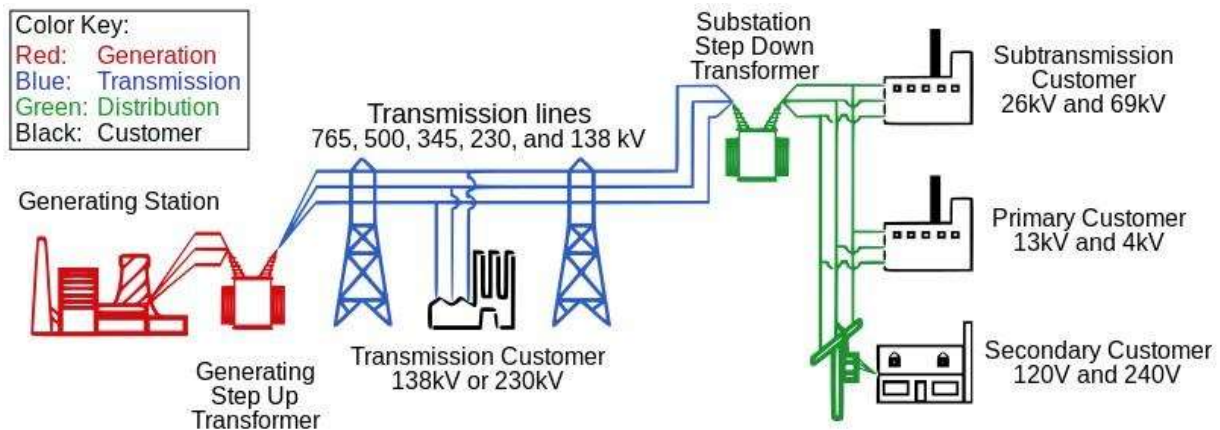
## Technology (old and new) & Main Characteristics Low Voltage, Medium Voltage, High Voltage



### Transmission Lines (High-Medium Voltage)

Transmission lines are those responsible for bulk movement of electrical energy (from generating substation to some consumption but mainly a distribution substation). Mostly AC systems, mix between Meshed and Radial.


- HV(defined differently for different regions) is used to have lower losses (due to lower currents).
- Transmission lines are predominantly overhead lines (exceptions are underground lines used for urban areas or environmentally sensitive locations).
- Transmission is mainly 3-Phase AC although 1-Phase AC is sometimes used.
- HVDC is sometimes implemented for greater efficiency over very long distances (hundreds of kms), also submarine power cables and lastly, in the interchange of power between grids that are not mutually synchronized.

### Historically...

- In very early days, no transmission (DC & generation and loads located near each other). 19th 20th centuries saw a rapid industrialization of this power transmission system.
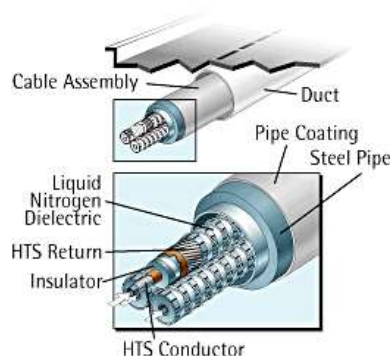
### What the future holds...

- High-temperature superconductors (HTS) promise to revolutionize power distribution by providing lossless transmission of electrical power. This would translate in having a "supergrid". This is a system based on an idea for combining very long electric power transmission with liquid nitrogen distribution, to achieve superconductivity in the power lines.



- HVDC as costs of inverters drop & interconnection between large power systems from different regions (no frequency differences) (other advantages include no reactive power).


- Wireless power transmission has been studied for transmission of power from Solar power systems to the earth. A high power array of microwave or laser transmitters would beam power to a receiver. This option presents a major challenge for engineering and presents a high level of uncertainty.

### Distribution Lines (Low Voltage)

Distribution lines are those involved in the final stage of electrical power delivery (from distribution substation to low voltage consumption)

- Almost always AC (excluding railway systems, telephone systems...).
- Meshed.
- Since 1880s (when electricity began being generated at power stations) and currently (in most places) it is a one directional power flow due to centralized generation.

### What the future holds...

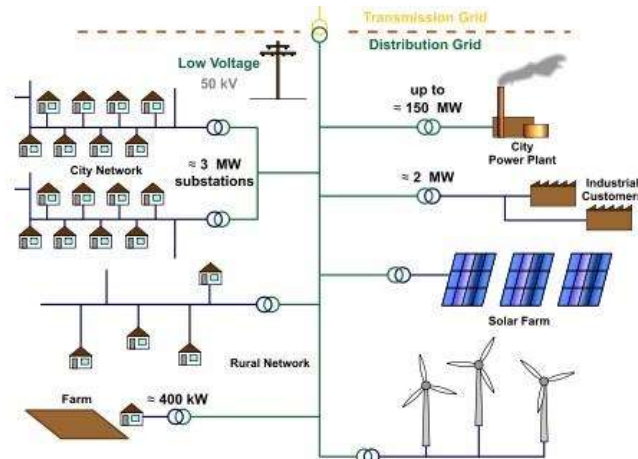

- Distributed generation presents a need for a two-directional distribution system: New regulation, smartgrids, storage (batteries, EVs), Voltage regulation capable of dealing with under and over voltage.



- DC (IF costs severely drop)

## Simulation: Voltage increase & checking different values of impedance in the lines

### Scaled Transmission Line (Laboratory)

#### Electric parameters

Frequency = 50 Hz

Voltage = 220 V

Current = 5 A

$$R = 1 \, \Omega, \quad L = 11 \, \text{mH}, \quad C = 2 \cdot 10^{-6} \, \text{F}$$

### Measures taken in the lab, feeding a variable load ( $\cos \varphi = 1$ )

```
clear all
% LECTURAS
V_inicial = [ 222 221 221 221 222 222 ]; % V
V_final   = [ 224 216 208 199 190 182 ]; % V
Pot       = [ 0 1 2 3 4 5 ]*1000; % W
```

Now, the  $R_{load}$  for each power consumption point measure is calculated.

$$R_{load}^{(i)} = \frac{(U_{load}^{(i)})^2}{P_{load}^{(i)}} \, (\Omega)$$

```
% Resistencia de carga
R_load = [];
for i = 1:length(V_final)
```

```
R_load(i) = V_final(i)^2/Pot(i);
end
```

### Base Magnitudes of the Line to calculate *per unit* measures

```
frecuencia = 50;
omega = 2*pi*frecuencia;

% Magnitudes base de la línea
U = 220;
I = 5;
S = sqrt(3)*U*I;
Z = U^2/S;

% Parámetros eléctricos de la línea
R = 1;
L = 11e-3;
C = 2e-6;

% Parámetros en p.u.
r = R/Z;
x = omega*L/Z;
b = omega*C*Z;
r_load = R_load/Z;


% Medidas en p.u.
v_inicial = V_inicial/U;
v_final = V_final/U;
```

### Voltage Drop ( $\Delta V$ ) vs. Power Consumption ( $P_{load}$ )

```
deltaV = (V_inicial - V_final)/(U);
pot = Pot/S;

% Ajuste de puntos
p = polyfit(pot,deltaV,2);
x1 = linspace(0,max(pot));
y1 = polyval(p,x1);

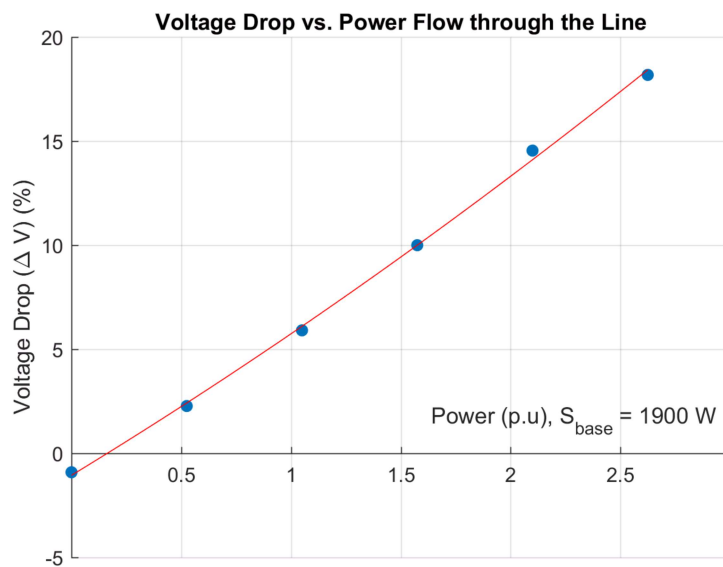ax = gca;
scatter(pot,deltaV*1e2,'fill');
hold on
plot(x1,y1*1e2,'r');
ax.XAxisLocation = 'Origin';
xlabel('Power (p.u), S_{base} = 1900 W ');
ylabel('Voltage Drop (\Delta V) (%)');
grid on
title('Voltage Drop vs. Power Flow through the Line');
```



### Modelling 132 kV, 100 MVA, 60 km Transmission Line

Now, once we have per unit parameters from the line in the lab, we re-scale them to the real 132 kV, 100 MVA, 60 km length transmission

line obtaining the next electric parameters.

```
% PARÁMETROS
Ubase = 132e3/sqrt(3);
Sbase = 100e6/3;
Ibase = Sbase/Ubase;
Zbase = Ubase^2/Sbase;

L = 60; % km
R = r*Zbase;
X = x*Zbase;
B = b/Zbase;

Z = (R + j*X);
Y = j*B;
R_load = r_load*Zbase;
Pot = pot*Sbase;

V_inicial = v_inicial*Ubase;
V_final = v_final*Ubase;
I_load = V_final./R_load;
deltaV_lab = V_inicial - V_final;
```

The electric parameters of the 132 kV transmission line are:

$$R = 6.86 \, \Omega \quad \chi = 23.70 \, \Omega \quad B = 3.05 \cdot 10^{-5} \, \Omega^{-1}$$

```
% Impedancia serie y admitancia paralelo
Zs = Z/L; % Ohm/km
Yp = Y/L; % S/km
```

Referring them to the length of the line, we obtain:

$$R = 0.114 \, \frac{\Omega}{km} \quad \chi = 0.3950 \, \frac{\Omega}{km} \quad B = 1.53 \cdot 10^{-6} \, \frac{1}{\Omega \cdot km}$$

Then, the propagation constant  $\gamma = \sqrt{Z_s \cdot Y_p}$  and the characteristic impedance  $Z_c = \sqrt{\frac{Z_s}{Y_p}}$  are calculated as follows:

```
% Constante de Propagacion
gamma = sqrt(Zs*(Yp));
gamma_A = sqrt(Zs*(Yp*1e6))% mrad/km
```

```
gamma_A =
    0.1112 + 0.7845i
```

```
lambda = 2*pi*1e3/imag(gamma_A) % km
```

```
lambda = 8.0087e+03
```

```
v = lambda*frecuencia/3e8 % m/s
```

```
v = 0.0013
```

```
% Impedancia caracteristica
Zc = sqrt(Zs/Yp)
```

```
Zc =
    5.1386e+02 - 7.2854e+01i
```

```
abs(Zc)
```

```
ans = 519.0009
```

### Characteristic Power of the line

It is possible to calculate the characteristic power of the line as follows:

$$P_c = \frac{U_c^2}{|Z_c|}$$

```
Pc = Ubase^2./abs(Zc)*1e-6
```

```
Pc = 11.1907
```

### Distributed Parameters Model

The calculation of Voltage and Current at the end of the line is made using the transfer matrix of distributed parameters for long transmission lines (line length bigger than 10 km).

$$\begin{bmatrix} V_l \\ I_l \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_o \\ I_o \end{bmatrix} = \begin{bmatrix} \cosh(\gamma L) & -Z_c \sinh(\gamma L) \\ -\frac{\sinh(\gamma L)}{Z_c} & \cosh(\gamma L) \end{bmatrix} \begin{bmatrix} V_o \\ I_o \end{bmatrix}$$

```
% Modelo Real de parametros distribuidos
% Elementos de la matriz de transferencia (A,B,C,D)
A = cosh(gamma*L);
B = -Zc*sinh(gamma*L);
C = -sinh(gamma*L)/Zc;
D = cosh(gamma*L);
M = [A B;
     C D]
```

```
M =
    0.9989 + 0.00031i   -6.8540 -23.6949i
    0.0000 - 0.00011i    0.9989 + 0.00031i
```

## Voltage drop simulation: Voltage at the begginig $V_o$

**First hypothesis.** The input data for voltage drop simulation are the current feeding the load  $I_{load}$  and the voltage in the load  $V_{load}$ . Then, changing the load (current at the end of the line), we obtain the different values of voltage drop depending on the power flow through the line.

$$\begin{bmatrix} V_o \\ I_o \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix}^{-1} \begin{bmatrix} V_l \\ I_l \end{bmatrix}$$


```
Io = [];
Vo = [];
for i = 1:length(V_inicial)
    V0 = inv(M)*[V_final(i); I_load(i)];
    Io(i) = V0(2);
    Vo(i) = V0(1);
end
Vo
```

```
Vo =
    1.0e+04 *

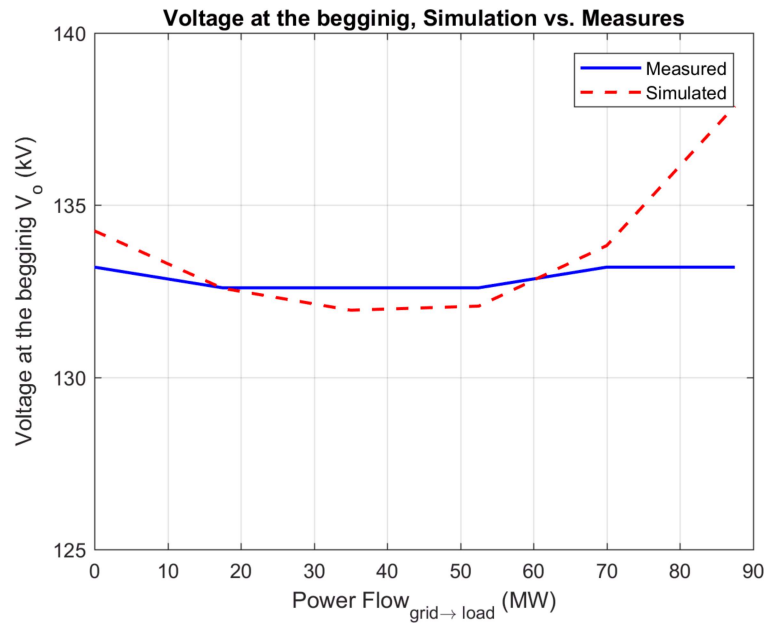    7.7512 + 0.0024i    7.6346 + 0.5564i    7.5304 + 1.1529i    7.4079 + 1.8063i    7.3034 + 2.5215i    7.2488 + 3.2896i
```

After that, we plot the Voltage at the begginig of the line versus the power flow through the line.


```
figure(2)
% Tension inicial medida
p1 = plot(Pot*1e-6,sqrt(3)*abs(V_inicial)*1e-3,'b','LineWidth',1.5);
grid on
xlabel('Power Flow_{grid\rightarrow load} (MW)')
ylabel('Voltage at the begginig V_o (kV)')
title('Voltage at the begginig, Simulation vs. Measures')
ylim([125 140])
hold on
% Tensión incial simulación
p2 = plot(Pot*1e-6,sqrt(3)*abs(Vo)*1e-3,'r--','LineWidth',1.5);
legend([p1;p2],'Measured','Simulated');
```



If we analyze the voltage drop we obtain for every load point:

$$\Delta V^{(i)} = V_o^{(i)} - V_f^{(i)}$$
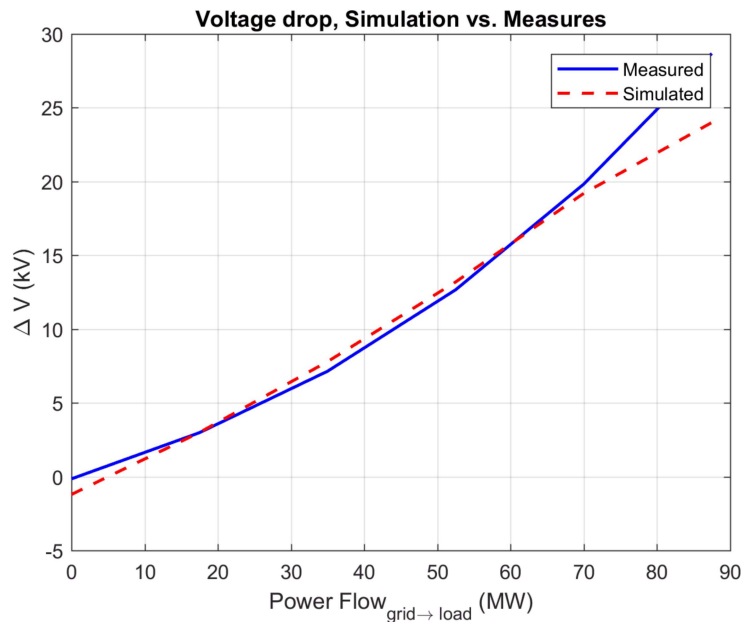
```
figure(3)
deltav = abs(Vo) - abs(V_final);
deltav_lab = V_inicial - V_final;
p3 = plot(Pot*1e-6,sqrt(3)*deltav*1e-3,'b','LineWidth',1.5);
xlabel('Power Flow_{grid\rightarrow load} (MW)')
ylabel('\Delta V (kV)')
title('Voltage drop, Simulation vs. Measures')
grid on
hold on
p4 = plot(Pot*1e-6,sqrt(3)*deltav_lab*1e-3,'r--','LineWidth',1.5);
legend([p3;p4], 'Measured', 'Simulated')
```



### Voltage drop simulation: Voltage in the load

**Second hypothesis.** Now, the input data for voltage drop simulation are the current feeding the load  $I_{load}$  and the voltage at the beginning  $V_o$ . Then, changing the load (current at the end of the line), we obtain the different values of voltage drop depending on the power flow through the line.

$$I_o = \frac{(I_l - C \cdot V_o)}{D}$$

$$V_l = A \cdot V_o + B \cdot I_o$$


```
v1 = [];
```

```

Io = [];
for i = 1:length(V_inicial)
    Io(i) = (I_load(i) - C*V_inicial(i))/D;
    Vl(i) = A*V_inicial(i) + B*Io(i);
end

figure(4)
% Tension final medida
p1 = plot(Pot*1e-6,sqrt(3)*abs(V_final)*1e-3,'b','LineWidth',1.5);
grid on
xlabel('Power Flow_{grid\rightarrow load} (MW)')
ylabel('Voltage at the end V_l (kV)')
title('Voltage at the end, Simulation vs. Measures')
ylim([105 140])
hold on
% Tensión inicial simulación
p2 = plot(Pot*1e-6,sqrt(3)*abs(Vl)*1e-3,'r--','LineWidth',1.5);
legend([p1;p2],'Measured','Simulated');

```

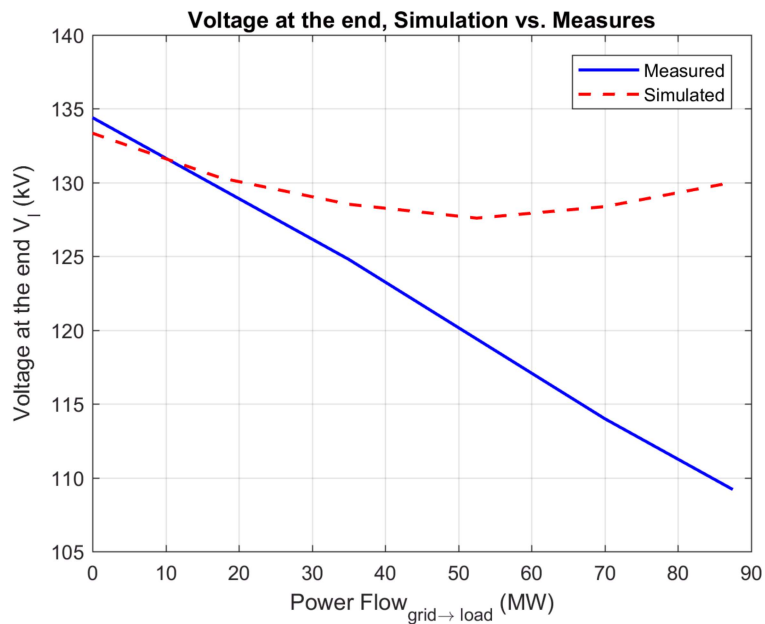


If we analyze the voltage drop we obtain for every load point:

$$\Delta V^{(i)} = V_o^{(i)} - V_f^{(i)}$$

```

figure(5)
deltav = abs(V_inicial) - abs(Vl);
deltav_lab = V_inicial - V_final;
p3 = plot(Pot*1e-6,sqrt(3)*deltav*1e-3,'r--','LineWidth',1.5);
xlabel('Power Flow_{grid\rightarrow load} (MW)')
ylabel('\Delta V (kV)')
title('Voltage drop, Simulation vs. Measures')
grid on
hold on
p4 = plot(Pot*1e-6,sqrt(3)*deltav_lab*1e-3,'b','LineWidth',1.5);
legend([p3;p4],'Simulated','Measured')

```

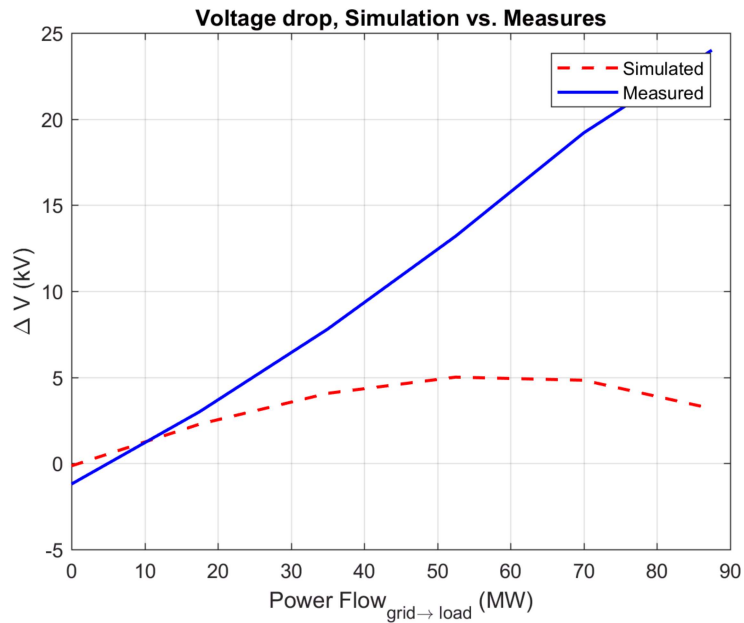

### Analysis of voltage drop in transmission lines with different $R/\chi$ relation.

In this section, some  $R/\chi$  medium voltage transmission lines are analyzed, working with different types of loads,  $\cos(\varphi) = 0.8$  ind, cap,  $\cos(\varphi) = 1$ .

$$\Delta U = r \cdot I \cdot \cos(\varphi) + \chi \cdot I \cdot \sin(\varphi)$$

$$\Delta U = \frac{1}{U} \cdot (r \cdot P + \chi \cdot Q)$$

```
k = 1;
r_l = [0.5 0.75 1 1.25 1.5 2]*k;
rel = [ 1 1.25 1.5 1.75 2 2.25];
% Long = [1 2.5 5 10 15 20]
R_tot = r_l;
X_tot = R_tot.*rel;
% Datos de entrada
U_n = 20e3/sqrt(3);
cosphi = 0.5:0.1:1;

S = 4e6/3;
P = S*cosphi;
Q = S*sin(acos(cosphi));
Q(1) = -Q(1); % cos capacitivo

for i = 1:length(R_tot)
    for j = 1:length(P)
        delta_u(i,j) = (1/U_n)*(R_tot(i)*P(j) + X_tot(i)*Q(j));
    end
end
delta_u
```

```
delta_u =
-21.1325    80.8290    81.6456    80.8290    77.1276    57.7350
-50.4487   138.5641   137.9300   134.2339   125.1288    86.6025
-92.2650   207.8461   204.5222   196.2991   179.4214   115.4701
-146.5812   288.6751   281.4222   267.0245   240.0056   144.3376
-213.3975   381.0512   368.6299   346.4102   306.8813   173.2051
-334.5299   554.2563   532.7376   496.5212   434.3411   230.9401
```

### Plotting simulation results


```
figure
for i = 1:6
    hold on
    op(i) = plot(cosphi,delta_u(i,:)*1e-3);
    xlabel('cos(\phi)');
    ylabel('Voltage Drop \Delta V (kV/km)')
    grid on
end
ax = gca;
ax.XAxisLocation = 'Origin';
```



```

title('Voltage drop vs. cos(\phi) for different R/\chi')
% xlabel('Length (km)')
% ylabel('Voltage Drop \Delta V (V)')
legend( [ op ], 'R/\chi = 1', 'R/\chi = 1.25', 'R/\chi = 1.5', 'R/\chi = 1.75', 'R/\chi = 2', 'R/\chi = 2.25', 'Location', 'South');

```

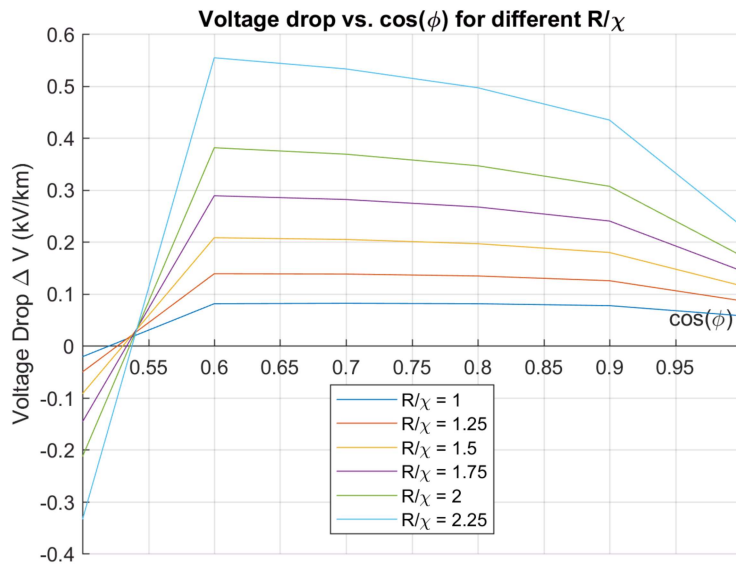

### Load working as generator. Voltage drop.

In this section, we assume that the load turn into generator, injecting power in 132 kV voltage level, connected to an infinite grid.

$$V_o = \frac{V_l - B \cdot I_o}{A}$$

$$I_l = C \cdot V_o + D \cdot I_o$$

```

R_load = r_load*Zbase;
I_load = Ubase./R_load;
Ip = [];
Vo = [];
for i = 1:length(I_load)
    Vo(i) = (Ubase - B*I_load(i))/A;
    Ip(i) = C*Vo(i) + D*I_load(i);
end
volt = Vo;

```

### Plotting results


```

t = [ Ubase Ubase Ubase Ubase Ubase Ubase ];
deltav = -abs(Ubase)+ abs(volt);

% Drop Voltage axis
figure
yyaxis left
p5 = plot(Pot*1e-6,sqrt(3)*deltav*1e-3,'LineWidth',1.5);
xlabel('Power Flow_{gen\rightarrow grid} (MW)')
ylabel('\Delta V (kV)')
title('Voltage drop, Simulation vs. Measures')
grid on
hold on

% Voltages axis
yyaxis right
p6 = plot(Pot*1e-6,sqrt(3)*abs(volt)*1e-3,'LineWidth',1.5);
xlabel('Power Flow_{gen\rightarrow grid} (MW)')
ylabel('V_{gen}, V_{grid}(kV)')
hold on
p7 = plot(Pot*1e-6,sqrt(3)*Ubase*1e-3 + Pot-Pot,'--','LineWidth',1.5);
title('Voltage increase \Delta V = V_{grid} - V_{gen} vs. Power Generated')
legend( [ p5; p6; p7 ], '\Delta V', 'V_{gen}', 'V_{grid}', 'Location', 'NorthWest');

```

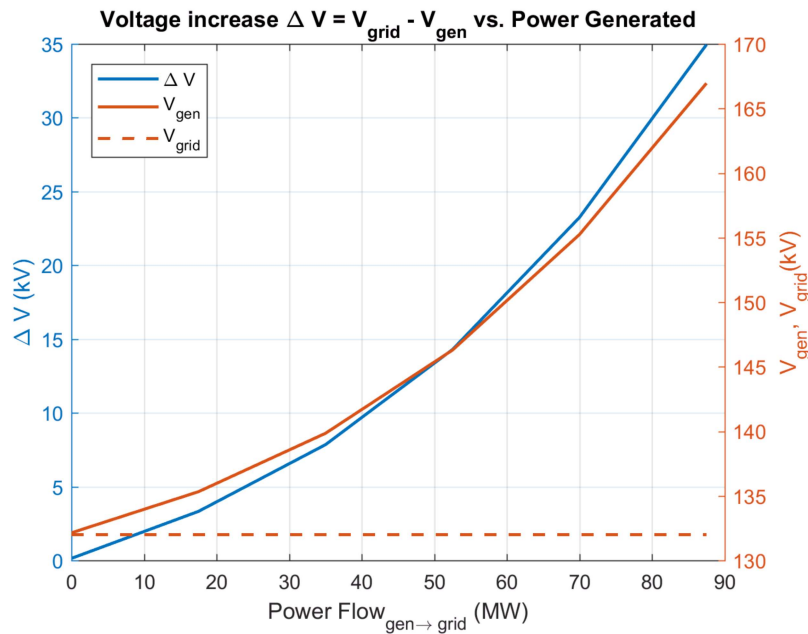

## Conclusions

### Conclusions from tests and simulations:

#### According to Distributed Parameters Modell in this case:

- It behaves properly when it comes to modell voltage and current at the beginning of the line from the ones at the end.
- It does not fit so well when we have mixed input (Voltage at the beggining and current in the load).
- We have found some mistakes that differ a lot from actual lines in the propagation constant  $\gamma$ , because the speed of propagation is too low in comparison with  $c$  and what it is common to find in overhead power lines (speed closed to  $c$ ).
- We assume it has to do with Capacitance between lines. A improvement must be done in modelling this electric parameter, whose influence has a determinant role in the rest of the model. (Transfer Matrix, Characteristic Impedance, Reactive Power Losses and Generation).

### General Solutions:

- Compensating with Capacitors, which reduce the voltage drop along the feeder by reducing current flow to loads consuming reactive:

### Power Factor ( $\cos(\varphi)$ ) Compensation.

```
S_loss = 3*(Vo.*conj(Io) - V_final.*conj(I_load))*1e-6;
Q_loss = imag(S_loss)
```

```
Q_loss =
    -1.6136    2.3262    16.0892    43.9277    91.4623   163.9248
```

```
ang = angle(S_loss(2:6))*180/pi;
j = 1;
w = 1;
for i = 1:length(Q_loss)
    if Q_loss(i) < 0
        Q_L(j) = Q_loss(i);
        j = j + 1;
    else
        Q_C(w) = Q_loss(i);
        w = w + 1;
    end
end
Q_L = Q_loss(1);
L = -Ubase^2/(omega*Q_L*1e6);
Q_C = Q_loss(2:6);
```

Different Capacities obtained to compensate the power factor depending on the power flow injected in the grid are calculated as follows:


$$C = \frac{U^2}{\omega \cdot Q_{line}} (F)$$

```
C = Q_C*1e6./(omega*Ubase^2)*1e6
```

```
C =
    1.2749    8.8178   24.0748   50.1263   89.8397
```


```
figure
subplot(2,1,1,gca)
plot(cos(ang*pi/180),C,'LineWidth',1.5)
xlabel('cos(\phi)')
ylabel('C_{shunt} (\mu F)')
title('Capacity vs. power factor in the line')
set(gca,'XGrid','on','YGrid','on')
legend('C (\mu F)')

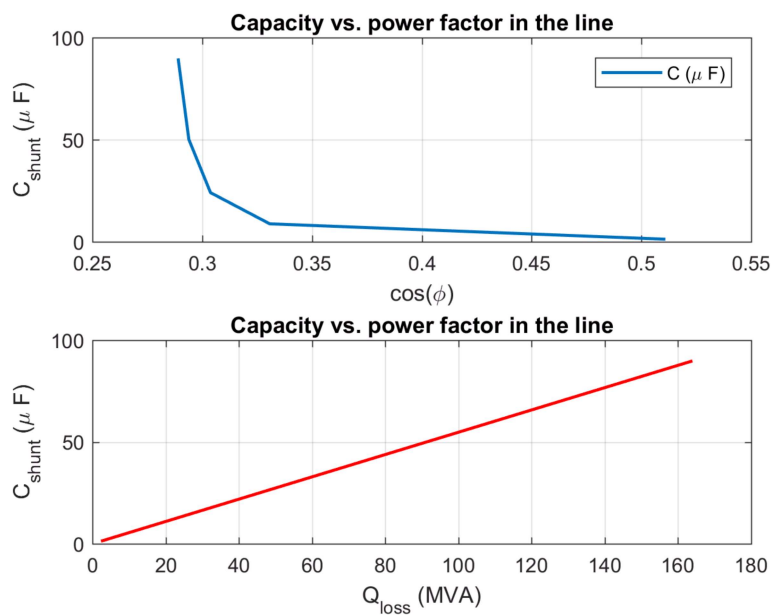subplot(2,1,2)
plot(Q_loss(2:6),C,'r','LineWidth',1.5)
xlabel('Q_{loss} (MVA)')
ylabel('C_{shunt} (\mu F)')
title('Capacity vs. power factor in the line')
grid on
```




- FACTS (Series, shunt):

#### FACTS en derivación

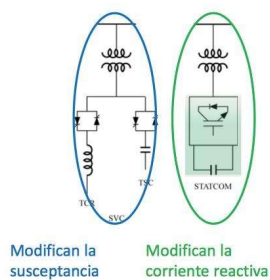

- Shunt FACTS are used to modify the susceptance and the reactive current.

#### FACTS en serie

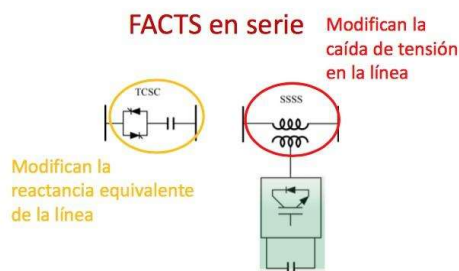

- Series FACTS are used to modify the reactance and therefore the impedance the line has in such a way that voltage can be controlled.

#### Voltage Regulators (Electronic, Electromechanic):

- Load tap changer (LTC) at the substation transformer, which changes the number of turns ratio in response to load current and

thereby adjusts the voltage supplied at the sending end of the feeder or voltage regulators, which are essentially transformers tap changers to adjust the voltage along the feeder, so as to compensate for the voltage drop over distance.

